

Name: _____

Date Started: _____ Date Completed: _____ Score: _____

Learning Activity Sheet

Circuit and Circuit Elements

Directions: Choose the letter of the correct answer and write it in the blank provided before each number.


For questions 1 and 2, refer to the diagram on the right.

_____ 1. What is the total resistance in the circuit?

- A. $8\ \Omega$
- B. $10\ \Omega$
- C. $12\ \Omega$
- D. $14\ \Omega$

_____ 2. What is the total current in the circuit?

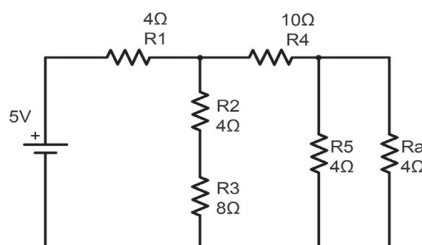- A. $0.2\ \text{A}$
- B. $0.3\ \text{A}$
- C. $0.4\ \text{A}$
- D. $0.5\ \text{A}$



_____ 3. What is the function of a switch?

- A. It provides voltage to the circuit.
- B. It provides electrical energy to appliances.
- C. It limits the total current passing through a circuit.
- D. It creates a short circuit or an open circuit, depending on its position.

_____ 4. Which device limits the total current passing from the transmission line into the house?

- A. battery
- B. fuse
- C. resistor
- D. switch

_____ 5. What is the total resistance of a $4\text{-}\Omega$ resistor and a $6\text{-}\Omega$ resistor connected in parallel?

- A. $2.4\ \Omega$
- B. $4\ \Omega$
- C. $5.5\ \Omega$
- D. $10\ \Omega$

- _____ 6. Which of the following shows a proper way of handling electronic devices?
- A. Touch active wires during a flood.
 - B. Avoid touching wires on power poles.
 - C. Handle electronic devices with a wet hand.
 - D. You can plug as many appliances as you like into a circuit.
- _____ 7. Which of the following is equal to the total resistance of a pair of $1\text{-}\Omega$ resistors connected in series?
- A. $2\text{ }\Omega$, and when in parallel $0.5\text{ }\Omega$
 - B. $0.5\text{ }\Omega$, and when in parallel $2\text{ }\Omega$
 - C. $1\text{ }\Omega$, and when in parallel $0.75\text{ }\Omega$
 - D. $1\text{ }\Omega$, and when connected in parallel $2\text{ }\Omega$
- _____ 8. Which of the following is NOT a safety measure when handling electronic devices?
- A. You can still use broken or frayed wires.
 - B. Avoid sticking your fingers into an electrical outlet.
 - C. Do not handle electronic devices when your hands are wet.
 - D. Always unplug an electrical appliance before attempting to repair it.
- _____ 9. Which of the following is NOT true about series circuits?
- A. The current in the different parts of the circuit varies.
 - B. The total resistance is equal to the sum of the resistance of the different parts.
 - C. The total voltage is equal to the sum of the voltages across the different parts of the circuit.
 - D. The various components comprising the circuit are connected that the current flows through each circuit component.
- _____ 10. Which of the following is NOT correct about a parallel circuit?
- A. It is the most commonly used circuit.
 - B. The voltage in any part of the circuit is the same.
 - C. The total resistance is equal to the sum of the resistances.
 - D. One side of each component is connected to a common junction, and the other side is connected to another common junction.