

Name: \_\_\_\_\_  
 Date Started: \_\_\_\_\_ Date Completed: \_\_\_\_\_ Score: \_\_\_\_\_

### Learning Activity Sheet Series and Parallel Circuits

**A. Instruction.** Circle the letter of the correct answer.

1. Which type of circuit consists of only one pathway for electric current?
  - a. Open circuit
  - b. Parallel circuit
  - c. Series circuit
  - d. Short circuit
2. There are three bulbs connected to one another in a parallel circuit. What will happen to the brightness of the bulbs if two more bulbs are added to the same circuit?
  - a. All the bulbs will be busted.
  - b. All the bulbs will be brighter.
  - c. All the bulbs will be dimmer.
  - d. All the bulbs will remain the same.
3. There are four bulbs connected to one another in a series circuit. What will happen to the rest of the bulbs if one bulb got busted?
  - a. The rest of the bulbs will not light up.
  - b. The rest of the bulbs will still light up.
  - c. Only the bulbs farthest to the busted one will light up.
  - d. Only the bulbs nearest to the busted one will not light up.
4. How can you lessen the brightness of the bulbs connected in a series circuit?
  - a. Add more bulbs in the circuit.
  - b. Use shorter conducting wires.
  - c. Use thinner conducting wires.
  - d. Add more batteries to the circuit.
5. Which type of circuit consists of more than one pathway for electric current?
  - a. Open circuit
  - b. Parallel circuit
  - c. Series circuit
  - d. Short circuit

**B. Instruction.** Analyze each illustration of the circuit below. Identify if it is a **series circuit** or a **parallel circuit**.

